

# Design Methods of Modern Ultra-Low-Noise Synthesizers

This first article in a multi-part series on modern synthesizers describes basic phase-locked-loop operation along with various topologies.

Recent years have seen major changes in frequency-synthesis art. Ultra-low-noise discrete voltage-controlled oscillators (VCOs), the heart of low-noise synthesizers for decades, now find themselves being challenged by integrated VCOs. While the best discrete VCOs still achieve 20 to 30 dB of phase-noise superiority, integrated-circuit (IC) companies are conducting an asymmetric battle to dominate the market with full integration based not on the best VCO noise, but on architectural innovations that often render free-running VCO noise less important.

Such a goal is achieved by putting good VCOs on die, suppressing that noise down to a very low level via feedback, and then dividing down to the application band. The challenge that discrete VCO suppliers now face is to extend the outstanding phase noise they achieve in application bands to higher frequencies, where they also get the full architectural benefit of the latest synthesizer innovations.


This article, the first of a four-part series, will review modern advanced design methods. The next three articles will dive into noise, key parts and tools,

and examples. Longer and more complete versions of these articles will be published online.

 
## BASIC PLL OPERATION AND SECOND-ORDER NORMALIZED FORM

The standard second-order form of phase-locked-loop (PLL) design that's presented in most classic textbooks allows for approximate, but still useful, design and analysis equations, along with a simple description of loop operation (Fig. 1).

We are accustomed to thinking primarily of voltage and current as the feedback quantities. But in addition to those, the PLL treats phase and frequency as small-signal frequency-domain variables. When seeking lock over a wide frequency range, the modern phase/frequency detector (PFD) acts as a frequency detector to steer the VCO toward lock. As frequency converges, the loop transitions to a phase-locked mode where phase as a time difference between digital edges is driven to zero.



 1. This is a depiction of the second- and third-order charge pump PLL synthesizer (C1 = 0 for second-order). Frequency is set by firmware via the programmable R and N dividers.



2. Shown is open-loop gain and phase in the properly designed third-order PLL. The maximum phase is forced to occur at the loop bandwidth by the design.

Since frequency is the time derivative of changing phase ( $\omega = d\theta/dt$ ), phase is the integral of frequency. Thus, the VCO acts as an integrator of input voltage to output phase, which introduces  $-90$  degrees of phase shift. That's why its transfer function is in the form  $K_o/s$ . Here,  $K_o$  is given in units of rad/sec/volt. VCO datasheets will normally give  $K_o$  in units of MHz/V. To be clear in this article series, we will refer to the Hz/V form of  $K_o$  as  $K_{Hz}$ . The radian form will be referred to as  $K_o$ , i.e.,  $K_o = 2\pi K_{Hz}$ .

With the  $-90$  deg phase shift and the  $-180$  degrees of negative feedback, we are only allowed a maximum of 90 degrees of filtering phase shift before  $-360$  degrees total results in instability. We normally leave a minimum of 40 degrees of "phase margin" at the loop bandwidth. This margin comes from the zero introduced by resistor  $R_2$ , as without it the charge pump driving a capacitor would also be an integrator.

From basic analysis of the loop in Fig. 1, we may find  $R_2$  and  $C_2$  as:

$$C = \frac{K_o I_{pd}}{2\pi N \omega_n^2} = \frac{K_{Hz} I_{pd}}{N \omega_n^2} \quad (1)$$

$$R = \frac{4\pi N \omega_n \zeta}{K_o I_{pd}} = \frac{2N \omega_n \zeta}{K_{Hz} I_{pd}} \quad (2)$$

The term  $\omega_n$  is the "natural" frequency (settling "ring down" frequency). It's close to the open-loop bandwidth. The term  $\zeta$  is the "damping factor" and must be greater than zero for stability (usually set at 0.5 to 1.0). See the online version for a derivation of the above and a more complete description.

## THE THIRD-ORDER PASSIVE FILTER PLL

This third-order passive filter PLL is the simplest highly usable form. It's realized by adding another capacitor (Fig. 1). Introducing another filter pole will eventually cancel out the zero. This means that there will be a frequency where phase peaks and then declines (Fig. 2).

The loop filter impedance is:

$$Z(s) = \frac{1+sT_2}{sA_0(1+sT_1)} \quad (3)$$

A half page of circuit analysis will establish:

$$T_2 = R_2 C_2 \quad (4)$$

$$T_1 = \frac{R_2 C_2 C_1}{A_0} \quad (5)$$

$$A_0 = C_1 + C_2 \quad (6)$$

The open-loop gain function is given by (see figure for  $G$  and  $H$ ):

$$GH(j\omega) = \frac{K_d K_o}{-N} \frac{1+j\omega T_2}{\omega^2 A_0 (1+j\omega T_1)} \quad (7)$$

We know  $K_d$ ,  $K_o$ , and  $N$ , and choose loop bandwidth  $\omega_L$  and phase margin  $\phi_m$ . To find our three unknowns  $A_0$ ,  $T_1$ , and  $T_2$ , we need three equations. We get them from the magnitude of  $GH$  (which is 1 at  $\omega_L$ ), the phase of  $GH$  (which gives  $\phi_m$  at  $\omega_L$ ), and the derivative of the phase of  $GH$  with respect to  $\omega$  (which is zero at  $\omega_L$ ). This is the basic methodology referred to here as the modern technique.

The magnitude of  $GH$  is:

$$|GH(j\omega)| = \frac{K_d K_o}{NA_0 \omega^2} \sqrt{\frac{1+\omega^2 T_2^2}{1+\omega^2 T_1^2}} \quad (8)$$

At  $\omega = \omega_L$ , this magnitude is 1, and we have:

$$A_0 = \frac{K_d K_o}{N \omega_L^2} \sqrt{\frac{1+\omega_L^2 T_2^2}{1+\omega_L^2 T_1^2}} \quad (9)$$


The phase margin expressed as a positive number from 0 to 90 degrees is the difference between the open-loop phase and 180 degrees, which is:

$$\phi_m = \tan^{-1}(\omega_L T_2) - \tan^{-1}(\omega_L T_1) \quad (10)$$

Taking the derivative of phase margin with respect to variable frequency, and setting it to zero at  $\omega = \omega_L$ , gives:
 
$$\frac{T_2}{1+\omega_L^2 T_2^2} - \frac{T_1}{1+\omega_L^2 T_1^2} = 0 \quad (11)$$





4. This is the active fourth-order filter and fifth-order PLL, with option for fifth-order filter. This filter is referred to as a “slow slew” active filter, as the input RC reduces speed requirements. Bandwidth limits of the op amp may still make it advantageous to use the two-pole input filter option (see online version).

For transfer impedance  $Z(f)$  we find:

$$Z(s) = \frac{V_{out}}{I_{pd}} = \frac{1+sT_2}{sA_0(1+sT_1)(1+sT_3)(1+sT_4)} \quad (37)$$

An importance point is that  $T_4$  shall be the lowest frequency pole.

We also find:

$$A_0 = C_1 + C_2 \quad (38)$$

The open-loop gain as a function of  $j\omega$  is:

$$GH(j\omega) = \frac{K_d K_o}{-N} \frac{1+j\omega T_2}{\omega^2 A_0 (1+j\omega T_1)(1+j\omega T_3)(1+j\omega T_4)} \quad (39)$$

Using the magnitude function of the open-loop transfer function (1 at loop BW), we get:

$$A_0 = \frac{K_d K_o}{N \omega_L^2} \frac{\sqrt{1+\omega_L^2 T_2^2}}{\sqrt{(1+\omega_L^2 T_1^2)(1+\omega_L^2 T_3^2)(1+\omega_L^2 T_4^2)}} \quad (40)$$

In order to maintain one set of equa-

tions whether or not  $f_1$  or  $f_3$  is lower, we refer both higher-frequency poles to the lowest pole  $f_4$ .

To evaluate  $A_0$ , we need  $T_4$  and  $T_2$ ; then we use the selected pole ratios to get  $T_1$  and  $T_3$ . The exact equation is:

$$\phi_m = \tan^{-1}(\omega_L T_2) - \tan^{-1}(\omega_L T_4) - \tan^{-1}(\omega_L T_{14} T_4) - \tan^{-1}(\omega_L T_{34} T_4) \quad (41)$$

The max phase margin occurs at the peak of the phase-margin function, where we substitute  $\omega = \omega_L$  after taking the derivative in the first derivative test:

$$\frac{T_2}{1+\omega_L^2 T_2^2} - \frac{T_1}{1+\omega_L^2 T_4^2} - \frac{T_{14} T_4}{1+\omega_L^2 T_{14}^2 T_4^2} - \frac{T_{34} T_4}{1+\omega_L^2 T_{34}^2 T_4^2} = 0 \quad (42)$$

Now these two may be solved numerically for  $T_2$  and  $T_4$ , leading then to  $T_1$  and  $T_3$  via the selected pole ratios (usually around 0.5 for the lowest pole above  $f_4$  and 0.25 for the next pole relative to  $T_4$ ). The below approximations may be used as starting points for the numerical solutions, or as is.

$$\phi_m = \tan^{-1}\left(\frac{\gamma}{\omega_L T_4(1+T_{14}+T_{34})}\right) - \tan^{-1}(\omega_L T_4) - \tan^{-1}(\omega_L T_{14} T_4) - \tan^{-1}(\omega_L T_{34} T_4) \quad (43)$$

We may use  $\gamma = 1$  or alter the value from 1 based on the optimization criteria in Banerjee (Ref. 2, 5<sup>th</sup> ed., chapter 36). The only variable remaining is  $T_4$ , which may be solved numerically, or approximately:

$$T_4 \cong \frac{1}{\omega_L} \frac{\cos \phi_m - \tan \phi_m}{(1+T_{14}+T_{34})} \quad (44)$$

If the approximate form is used, then:

$$T_2 \cong \frac{\gamma}{\omega_L^2 (T_1+T_3+T_4)} \quad (45)$$

In either case:

$$T_1 = T_{14} T_4 \quad (46)$$

$$T_3 = T_{34} T_4 \quad (47)$$

We now have all of the variables needed to find  $A_0 = C_1 + C_2$ . We may then find all of the part values in  $Z_{for}$  from:

$$C_1 = \frac{T_1 A_0}{T_2} \quad (48)$$

$$C_2 = A_0 - C_1 \quad (49)$$

$$R_2 = \frac{T_2}{C_2} \quad (50)$$

Now we select the values for  $R_3$ ,  $C_3$ ,  $R_4$ , and  $C_4$ , which seems easy as we have their time constants. But there are some subtle complexities at work here, including op-amp limits to consider.

On the input side of the op amp, it might seem like a smaller  $R_3$  would help with noise. However, the opposite is actually true. The thermal noise of  $R_3$  rises proportionally with its square root. But as  $R_3$  increases, the noise gain decreases. Therefore, the noise of  $R_3$  on the op-amp output decreases with its square root. So, we tend to select the

largest  $R_3$  that other limits allow, as follows.

Banerjee gives (Ref. 2, 5<sup>th</sup> ed, p.38) the duty cycle of the phase-frequency detector in frequency-lock mode as a function of the ratio of  $f_{ref}$  and  $f_{out}/N$  as:

$$D_c = 1 - \frac{f_{lower}}{f_{upper}} \quad (51)$$

In the above,  $f_{lower}$  is the smaller of  $f_{ref}$  and  $f_{out}/N$ . Since most VCOs do not steer far in a fractional sense from their center frequency, the duty cycle would seldom range above 10% (octave-type VCOs being the exception).

Let us define  $\Delta V_{mC3}$  as the max filtered voltage change from  $V_{ref}$  that we wish to be imposed (such as to comply with op-amp input requirements) on  $C_3$  during a frequency-lock acquisition event. We may thus write a relationship for  $R_{3max}$  as:

$$R_{3max} = \frac{\Delta V_{mC3}}{D_c I_{pd}} \quad (52)$$

In addition, we need to beware of slew-rate limits. Banerjee offers experimental evidence (Ref. 2, 5<sup>th</sup> ed., pp. 371-372) that if the op amp is not fast enough, there will be worsening of 1/f phase noise inside the loop bandwidth (typically a few dB). Four slew rate cases are derived in the online version: two in frequency-acquisition mode (for lock speed) and two in PLL mode (for noise control). The worst case (highest

requirement on slew rate is usually the frequency-locking case toward the end of the frequency-lock process given by:

$$\text{ReqSlewRateFLL}(R_2 \text{ limited}) \cong \frac{D_{cmax} I_{pd}}{C_3} \frac{R_2}{R_3} \quad (53)$$

Additionally, bandwidth limits of the op amp are an issue. However, this can be mitigated by the two-pole input filter option. This allows the op amp to be “cocooned” within filtering that prevents signals beyond its specified bandwidth from reaching it. This would seem to be a more logical strategy than the typical  $GBW > 10X$  loop bandwidth that’s often assumed with op-amp circuits. See the online version for further discussion.

Next, we consider the op-amp output current limits on  $C_4$ . We are used to seeing strict limits on op amps, but against a capacitor (not a pure dc load), many can drive loads of 10  $\Omega$  and sometimes even less. But, with a large frequency change on the PLL, that capacitance does take large current that may exceed the op-amp max in the range of 10 to 100 mA. Fundamentally, we desire the op-amp max current  $I_{opmax}$  to be able to charge  $C_4$  at the same rate that  $D_c * I_{pd}$  charges  $C_2$  during a large frequency change. Using  $I * t = CV$ :

$$C_{4max} = \frac{I_{opmax} C_2}{D_c I_{pd}} \quad (54)$$

This maximum is sometimes more than we would like to use due to size and cost reasons, possibly leading to resistor values too small for the op amp. In that case, we select a value of  $R_4$  that allows for thermal noise considerably less than that of the op amp. We then find  $C_4 = T_4/R_4$ .

**WHAT'S NEXT**

The transfer-function approach presented here leads to noise sources and shaping in article 2 of the series, along with revealing the key innovations driving full integration and how discrete VCO makers can fight back. Article 3 will focus on key parts and CAD tools that are the weapons of the low-noise synthesizer designer. Article 4 will put it all together with requirements and examples of integrated and discrete VCO synthesizers to meet them. [mmw](#)

**ACKNOWLEDGMENTS**

The author expresses his appreciation for the valuable reviews, comments and information provided by Adnaan Khan, Joe Bouchez of LoneStar III Five Designs, Dean Banerjee at Texas Instruments, C.Y. Teng and Miguel Troester at Taitien, and Ulrich Rohde, Ajay Poddar, and Bill Becker at Synergy Microwave.

**REFERENCES**

1. “Digital PLL Frequency Synthesizers: Theory and Design”, Ulrich L. Rohde, Prentice-Hall, 1983.
2. “PLL Performance, Simulation, and Design”, Dean Banerjee, First Edition 1998. The 5th edition of 2017 of this outstanding reference may be freely downloaded at: [http://www.ti.com/tool/pll\\_book](http://www.ti.com/tool/pll_book).
3. “Phase-lock Techniques,” 2nd Ed, Floyd Gardner, John Wiley and Sons, 1979.
4. “Phase Locked Loops,” Third Edition, Roland Best, McGraw-Hill, 1997.

NEW ! NEW ! NEW !

We stock the new rugged **FRAMES CALLI** 100W transistor and parts for the 200 and 50-100MHz amplifier designs.



**RF Amplifiers**  
We stock the complete 100W and 50W transistor for the FRAMES CALLI 100W Amplifier designs and Engineering Solutions



**RF Transistors**  
100W 100MHz  
50W 100MHz



**RF Transformer**  
Type "A"  
100W 100MHz



**HF Power Amplifier / Combiner**  
2 to 50MHz



**CCI Communication Concepts, Inc.**  
[www.cci-communication.com](http://www.cci-communication.com)

500 Millstone Drive,  
Darrowood, OH 44024-0040  
Email: [vol@ccicom.com](mailto:vol@ccicom.com)  
Phone (440) 429-0000  
FAX (440) 429-0011

**2 Post**  
P8-2 100W P1P  
P8-2A 100W P1P

**4 Post**  
P8-4 100W P1P  
P8-4A 100W P1P  
P8-4B 100W P1P